

# MIT Art's, Commerce, Science College Alandi (D)

## F. Y. B.Sc. (Computer Science) Question Bank Electronic Device, Circuits & Computer Peripherals (Electronics-1)

By- Prof. Mr.S.P.Mahjan.

### Chapter 1. DC- Circuit Analysis

Q.1 State the following theorems:

1) Norton 2) Thevenins 3) Superposition

Q.2 State Kirchoff's voltage & current laws.

Q.3 Explain KCL & KVL. Give formulas of  $I_b$ ,  $I_c$  &  $I_e$ .

Q.4 Draw the Thevenins equivalent circuit.

Q.5 Draw the Norton equivalent circuit.

Q.6 Draw & state the superposition theorem.

Q.7 State Ohm's law.

Q.8 What is the equivalent resistances of three resistances  $R_1$ ,  $R_2$  &  $R_3$  in series & parallel.

Q.9 What is the equivalent Capacitances of three capacitor  $C_1$ ,  $C_2$  &  $C_3$  in series & parallel

### Chapter 2. Semiconductor Diode

Q.1 Draw the symbols of the following:

1. Rectifier Diode
2. LED
3. Photodiode
4. Zener Diode

Q.2 What do you mean by forward bias & reverse biased with respect to diode?

Q.3 Draw I-V characteristics of diode.

Q.4 What is photodiode?

Q.5 What is opt coupler?

Q.6 State two types of seven segment LED display.

Q.7 Explain the formation of P-N diode. Define depletion region & barrier potential.

Q.8 Draw I-V characteristics for Zener diode. Explain Zener breakdown & avalanche breakdown.

Q.9 “LED emits light in forward bias but diode doesn’t” comment.

### Chapter 3. Bipolar Junction Transistor

Q.1 Why is BJT known as bipolar transistor.

Q.2 Draw the symbol for NPN & PNP transistor.

Q.3 What is Q-point of a transistor.

Q.4 Draw the DC load line for CE amplifier & show saturation, active & cut off regions on the load line.

Q.5 Explain the action of NPN transistor with neat diagram .

Q.6 How transistor works as a switch.

Q.7 For certain transistors  $\alpha = 0.96$  &  $I_E = 4\text{mA}$ . Calculate  $I_C$  &  $I_B$ .

Q.8 Explain Q point for the transistor circuit. Draw DC load line.

Q.9 A silicon transistor has a collector cut off current as  $14\mu\text{A}$  at room temperature &  $\beta = 50$ . What is the collector current when the base current is  $0.2\text{mA}$ ?

### Chapter 4. Field Effect Transistor

Q.1 Compare FET & BJT.

Q.2 Why is FET called a unipolar transistor.

Q.3 Define the following parameter:

1. DC drain resistance
2. Trans conductance
3. Amplification factor

Q.4 State various advantages of JFET.

Q.5 Draw & explain MOS capacitor.

Q.6 Explain working of DE-MOEFET.

Q.7 How can MOSFET be used as inverter.

Q.8 Draw drain & trans conductance characteristics DE-MOSFET & show depletion & enhancement mode.

Q.9 What are advantages of CMOS.

### Chapter 5. Amplifier

Q.1 Draw the block diagram of op-amp & explain.

Q.2 List at least five parameter of an ideal op-amp.

Q.3 Define the following parameter:

1. Input Impedance
2. Slew rate
3. Bandwidth
4. CMRR

Q.4 Give classification of amplifier based on Q point.

Q.5 Derive the equation for the gain of non-inverting op-amp.

Q.7 Define  $\alpha$  &  $\beta$ . Derive the relation between  $\alpha$  &  $\beta$ .

Q.8 Explain op-amp as an integrator & derive the output equation.

Q.9 Explain op-amp as a differentiator & derive the output equation.

### Chapter 6. Oscillator

Q.1 State Barkhausen criteria required for oscillations.

Q.2 With neat diagram explain the working of phase shift oscillator.

Q.3 Write a note on Colpitts oscillator.

Q.4 In Hartley oscillator  $L_1 = 1\mu\text{H}$ ,  $L_2 = 0.2\mu\text{H}$  &  $C = 1000\text{pF}$ . Calculate the frequency of oscillations.

Q.5 In phase shift oscillator  $R = 1.8\text{K}\Omega$ ,  $C = 10\text{pF}$ . Calculate the frequency of oscillations.

### Chapter 7. Power Supply

Q.1 Define unregulated & regulated power supply.

Q.2 Which device is used as a rectifier.

Q.3 Define line & load regulation with their ideal values.

Q.4 What is use of heat sink?

Q.5 What are advantages & disadvantages of SMPS?

Q.6 What is need of UPS?

Q.7 With block diagram explain on line UPS.

Q.8 Explain the use of spike protector.

Q.9 Compare half, full & bridge rectifier.

Q.10. Explain three pin positive & negative voltage regulator.

Q.11. Explain the working of SMPS with proper block diagram.

Q.12. Give any five specification of power supply.

Q.13. With block diagram explain off line UPS.

Q.14. What is Snubber?

Q.15. Compare ON line & OFF line UPS.

### Chapter 8. Electronics in computer system

Q.1 State main component present in the mother board.

Q.2 What are the different types of key boards? Give the main feature of windows keyboard.

Q.3 State the various types of mouse. Explain the mechanism of optical mouse.

Q.4 Explain the working of CCD camera.

Q.5 Explain the working principle of CRT monitor.

Q.6 What is LCD display. Explain plasma display.

Q.7 Explain the working of LASER printer & dot matrix.

Q.8 State the various types of output devices.

Q.9 What are the different types of ear phones. Explain any one.