



FACULTY OF ENGINEERING
B.E. 2/4 (CSE) I Semester (Supplementary) Examination, July 2010
BASIC ELECTRONICS

Time : 3 Hours]

[Max. Marks : 75

Note : Answer all questions from Part A. Answer five questions from Part B.

PART – A

25

1. What is diffusion current ? 3
2. What are the doping levels of a zener diode ? 2
3. Differentiate between an FET and a BJT. 3
4. What is Hall effect ? 2
5. How does the gain of an amplifier vary with feedback ? 3
6. Explain Barkhausen criteria. 2
7. Draw the VI characteristics of a DIAC. 3
8. Mention the ideal characteristics of an ideal op amp. 2
9. What is Early Effect ? 3
10. Enlist the various applications of CRO. 2

PART – B

50

11. a) Explain the Energy band diagram and Fermi level of an intrinsic and extrinsic semiconductor.
b) With neat sketches, explain the operation of a rectifier with capacitor filter.
12. a) Explain the construction and operation of a JFET. Derive the relationship between μ , g_m and r_d .
b) Draw the circuit of the common emitter and explain its n-parameter model.



13. a) Explain the operation of series and shunt regulators.
b) Explain the operation of a simple inverter circuit.
14. a) What are the advantages of negative feedback ?
b) Compare between oscillator types.
15. a) Draw the functional block diagram of an op-Amp and explain the function of each block.
b) What are the basic logic gates ? Explain with truth tables.
16. a) Explain the working of a UJT. What is intrinsic stand off ratio ?
b) Draw a neat labelled diagram of a CRO.
17. Write notes on :
 - a) TRIAC
 - b) Differentiator.

Handwritten signature