

Code No.: 209

FACULTY OF ENGINEERING

B.E. II/IV Year (CSE) I Semester (Supplementary) Examination,
May / June 2009

BASIC ELECTRONICS

Time : 3 Hours]

[Max. Marks : 75

Answer **all** questions from Part A.
Answer **five** questions from Part B.

Part - A (Marks : 25)

1. Define the terms :
 - (i) Mobility
 - (ii) Diffusion
 - (iii) Drift current.

3
2. Draw the circuit diagram of a bridge rectifier and explain its working.

3
3. Define μ , r_d , & g_m of an FET and show that $\mu = r_d \times g_m$

3
4. What is meant by the quiescent point of a transistor amplifier.

3
5. What is a load line? Explain its significance.

2
6. What are advantages of negative feedback.

2
7. What is the Barkhausen criterion ? State the basic conditions for oscillations in feedback amplifier.

2
8. Give the Boolean expressions for 'OR', 'AND' & 'NOT' functions.

2
9. Define CMRR and what is its importance in op-amp.

2
10. Draw the block diagram of a General purpose CRO and indicate its basic components.

3

Part - B (Marks : 50)

11. (a) Draw the circuit diagram of a HWR and explain its working and define I_{dc} , I_{rms} ripple factor & efficiency.

5
- (b) Qualitatively explain the existence of capacitance in a p n junction diode when it is forward biased and when it is reverse biased.

5

[P.T.O.]

12. (a) Define h – parameters of a BJT in CE configuration. How does these parameters change with temperature and biasing parameters ? Explain. 5
- (b) Draw the Schematic of P- channel JFET and explain the different regions in the static drain characteristics. How do you determine the JFET parameters (μ , r_d & g_m). 5
13. (a) Explain with the help of block diagram the working principle of a Feedback amplifier. Find out an expression for the voltage gain with feedback. 5
- (b) Draw the circuit diagram of Hartley oscillator and explain its working and give the expression for condition for oscillations and frequency of oscillations. 5
14. (a) Give the logical symbols, Boolean expressions and the truth tables of a two input NOR and two input NAND gate. 4
- (b) Explain how an op-amp can be used as summer, Integrator and voltage to current converter with the help of diagrams. 6
15. (a) In connection with a CRO, explain the following terms (i) Sweep voltage (ii) Synchronization (iii) Time base. 6
- (b) Explain the working of strain gauge with a neat diagram. 4
- 16.(a) Draw the structures of UJT and explain its principle of operations. Plot its characteristics and explain the significance of negative resistance. 5
- (b) Draw the circuit diagram of weins bridge oscillator and explain its operations. 5
- 17 (a) Explain how Zener diode can be used as a regulator what is meant by load regulation & line regulation. Explain. 5
- (b) Draw the full wave rectifier circuit with capacitor input filter and explain how ripple can be eliminated? Show the relevant wave forms with and without capacitor filter. 5